
```
崔浩然
<mark>2020302181062</mark>
```


EDA-3-6:

```
代码文件:
module mult4 (S0,S1,S2,S3,A,B,C,D,Y);
input S0,S1,S2,S3,A,B,C,D;
output Y;
reg Y;
always@(S0,S1,S2,S3,A,B,C,D)
begin
if (S0==0) Y=A;
if (S1==0) Y=B;
if (S2==0) Y=C;
if (S3==0) Y=D;
end
Endmodule
```

网表文件:

 

资源开销:

 

```
仿真文件:
`timescale 1 ps/ 1 ps
module mult4_vlg_tst();
// constants
// general purpose registers
reg A;
reg B;
reg C;
reg D;
reg SO;
reg S1;
reg S2;
reg S3;
// wires
wire Y;
// assign statements (if any)
mult4 i1 (
// port map - connection between master ports and signals/registers
    .A(A),
    .B(B),
    .C(C),
    .D(D),
    .SO(SO),
    .S1(S1),
    .S2(S2),
    .S3(S3),
    .Y(Y)
```

); initial begin

```
// insert code here --> begin
#0 A=1'b0;
#0 B=1'b0;
#0 C=1'b0;
#0 D=1'b0;
#0 S1=1'b0;
#0 S2=1'b0;
#0 S3=1'b0;
#0 S0=1'b0;
// --> end
$display("Running testbench");
end
always #1 A=~A;
always #2 B=~B;
always #3 C=~C;
always #4 D=~D;
always #5 S0=~S0;
always #6 S1=~S1;
always #7 S2=~S2;
always #8 S3=~S3;
always@(Y);
endmodule
```

// code that executes only once

仿真结果:

